

Tutorial on Modern Ultra Low Noise Microwave Transistor Oscillator Design

Columbia University
September 11, 2009

Ulrich L. Rohde, Ph.D.*

Chairman Synergy Microwave Corp.

*Prof. of RF Circuit and Microwave Circuit Design

Brandenburg University of Technology

Cottbus, Germany



Faculty 3
Mechanical Engineering,
Electronic Engineering
and Industrial Engineering





Brandenburg University of Technology Cottbus


Ulrich L. Rohde, Prof. Dr.-Ing. Dr. h. c. mult.
RF and Microwave Circuit Design Techniques

P.O. Box 10 13 44
03013 Cottbus
Konrad-Wachsmann-Allee 1
03046 Cottbus, Germany

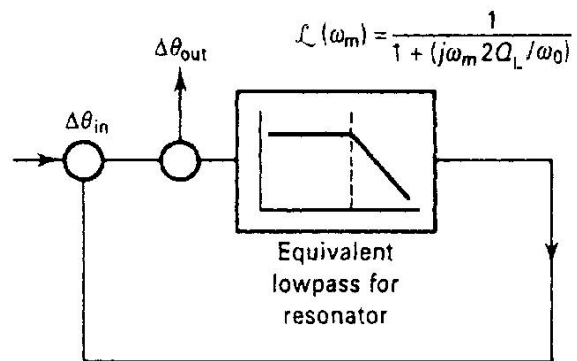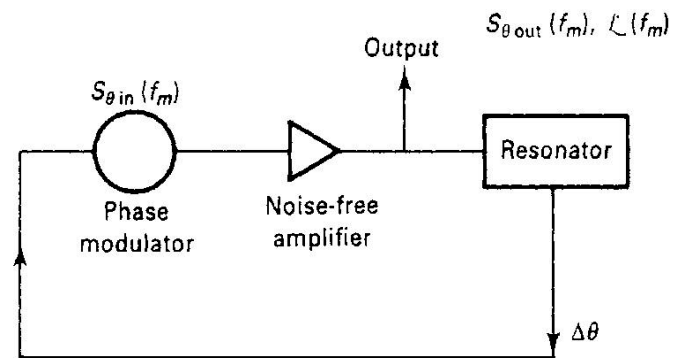
phone: +49 355 69-5062
fax: +49 355 69-2150
e-mail: rohdeu@tu-cottbus.de
www.kt.tu-cottbus.de



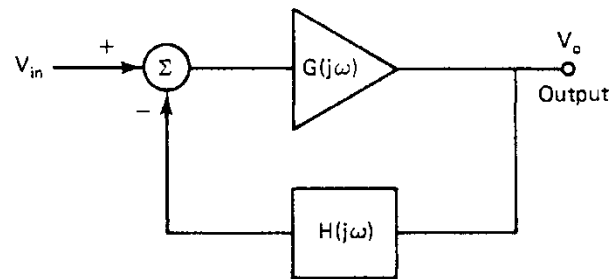A typical linear oscillator phase noise model (block diagram)
Leeson Model



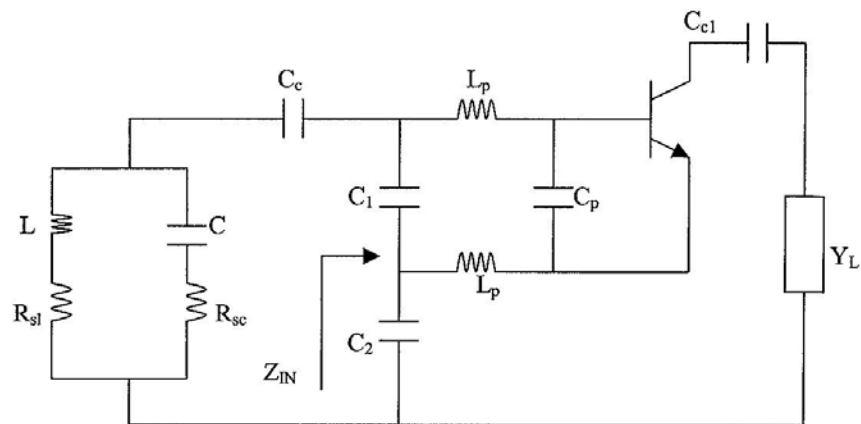A typical block diagram of feedback oscillator circuit





Colpitts oscillator with base-lead inductances and package capacitance. C_c is neglected.

The expression of input impedance is given as

$$Z_{IN}|_{package} = - \left[\frac{Y_{21}}{\omega^2 (C_1 + C_p) C_2} \frac{1}{(1 + \omega^2 Y_{21}^2 L_p^2)} \right] - j \left[\frac{(C_1 + C_p + C_2)}{\omega (C_1 + C_p) C_2} - \frac{\omega Y_{21} L_p}{(1 + \omega^2 Y_{21}^2 L_p^2)} \frac{Y_{21}}{\omega (C_1 + C_p) C_2} \right]$$

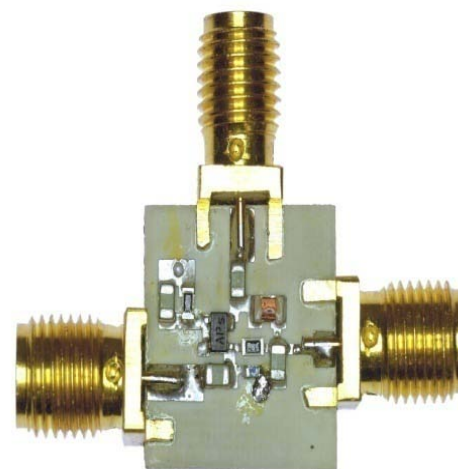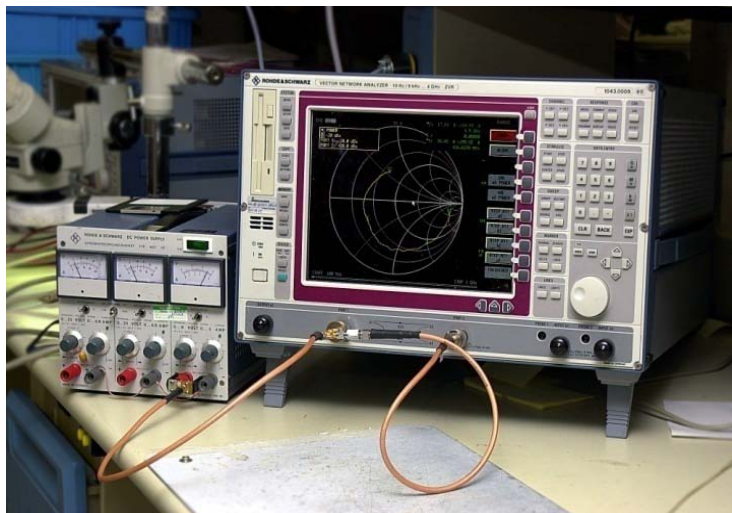
This Figure shows the R&S vector analyzer and the test fixture




Typical measurement setup for evaluation of large signal parameters (R&S vector analyzer and the test fixture for the transistor of choice)

Agilent now calls this X Parameters

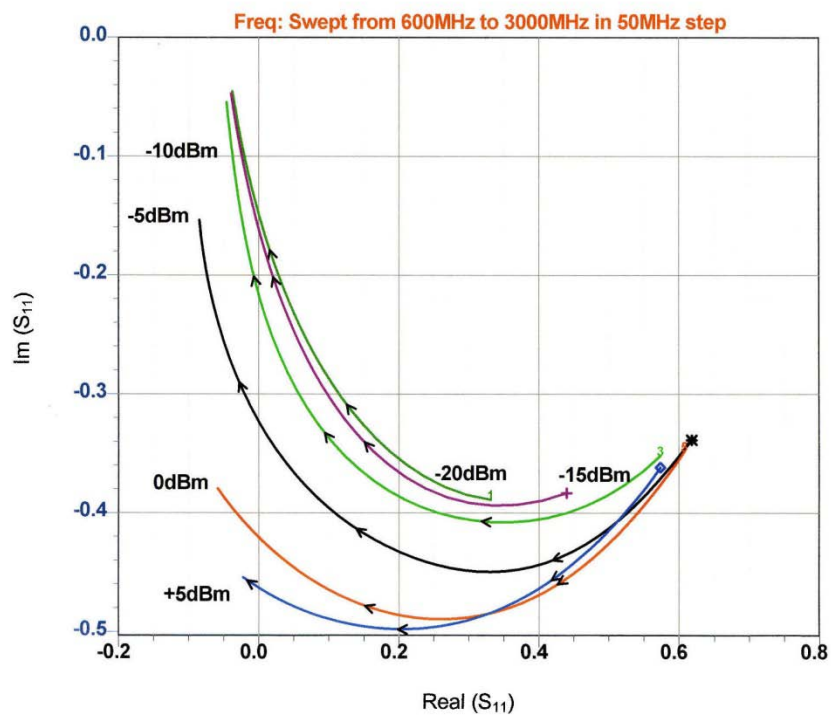
The bias, drive level, and frequency dependent S parameters are then obtained for practical use.



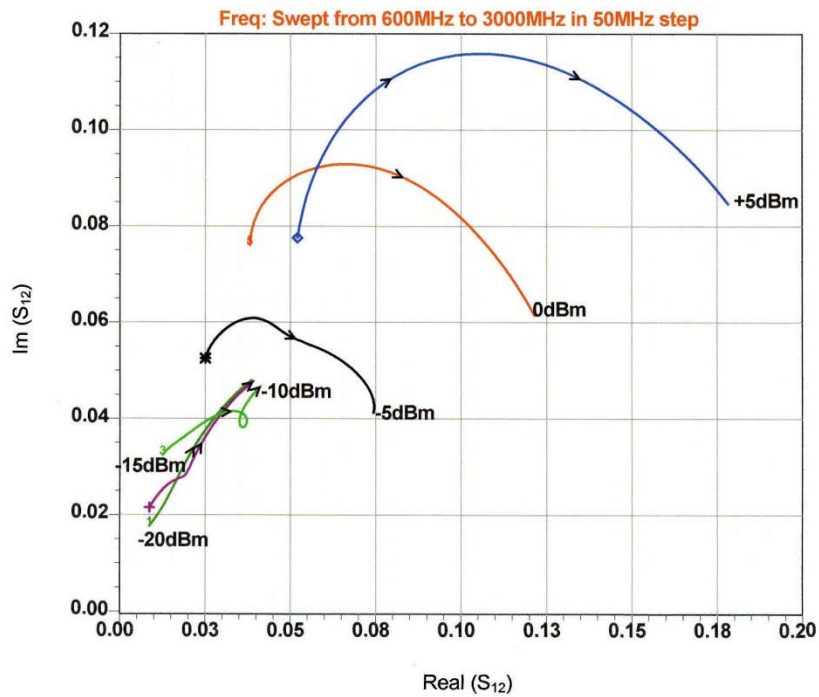
Measured large-signal S_{11} of the BFP520



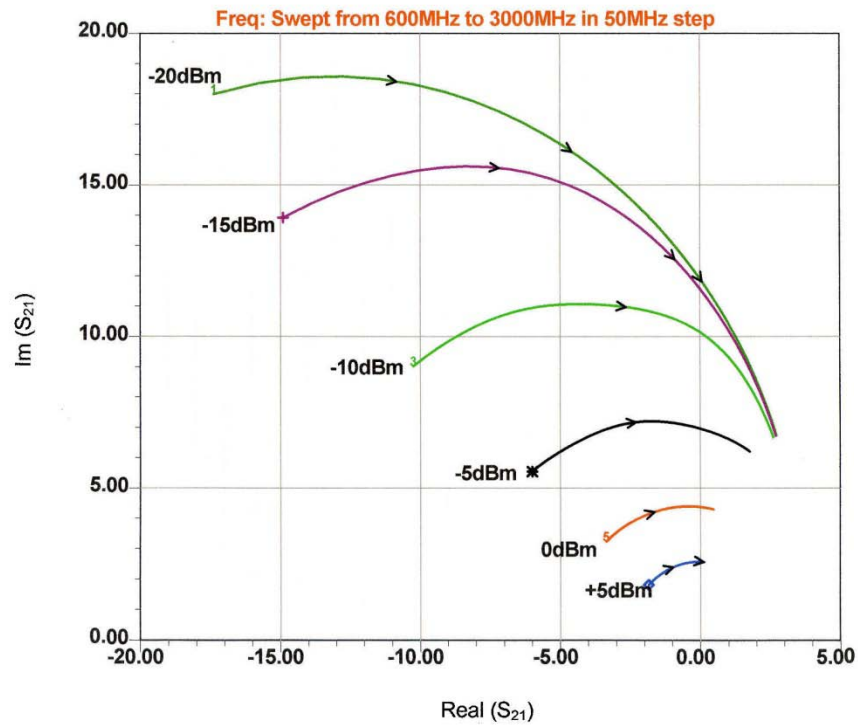
Measured large-signal S_{12} of the BFP520



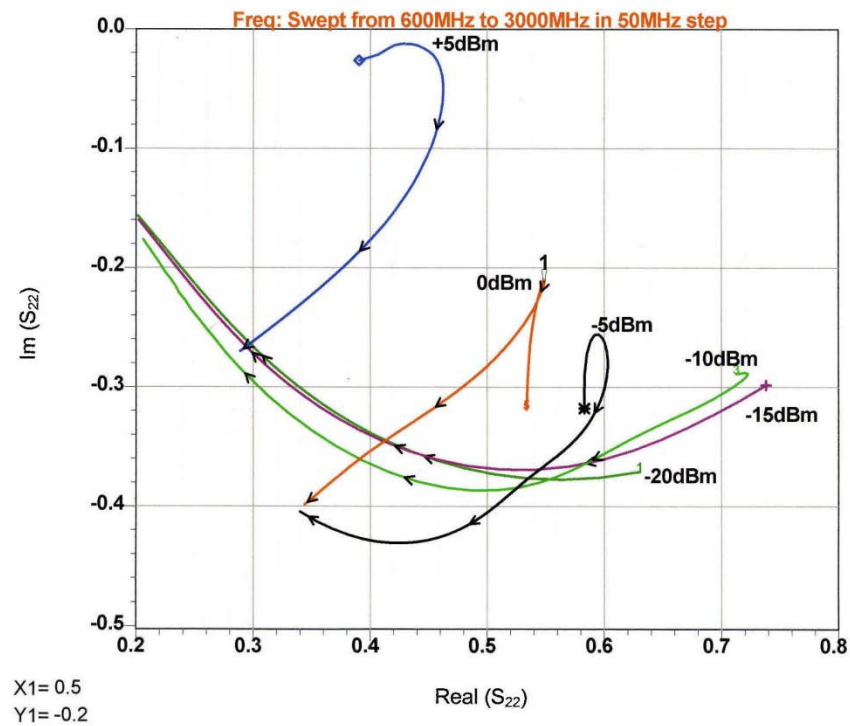Measured large-signal S_{21} of the BFP520




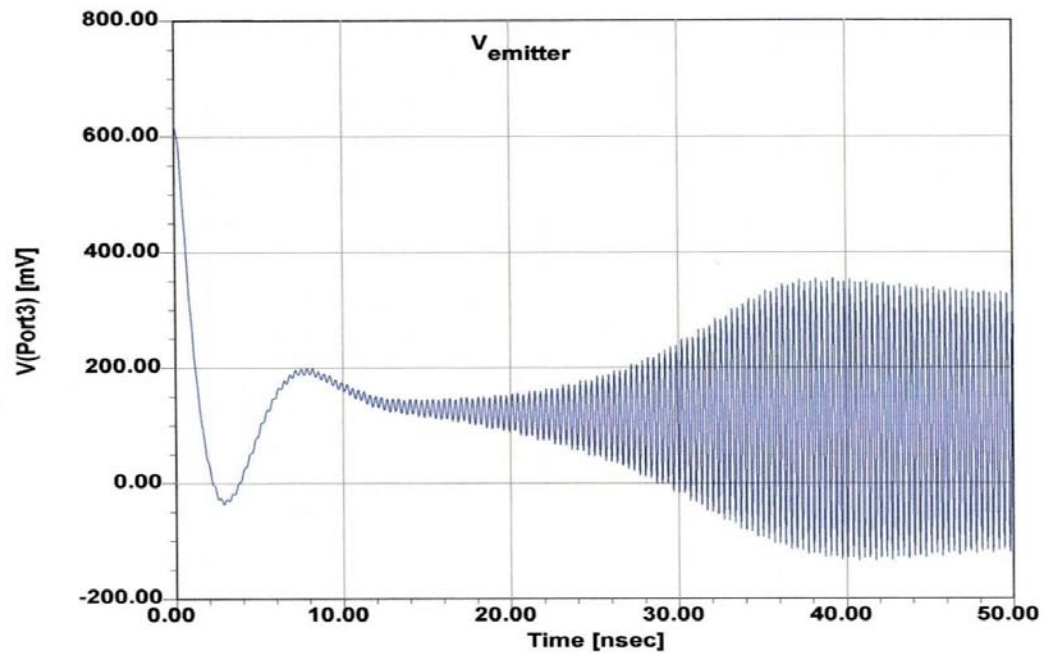Measured large-signal S_{22} of the BFP520



Typical transient simulation of a ceramic resonator-based high-Q oscillator (node of the voltage for display is taken from the emitter)

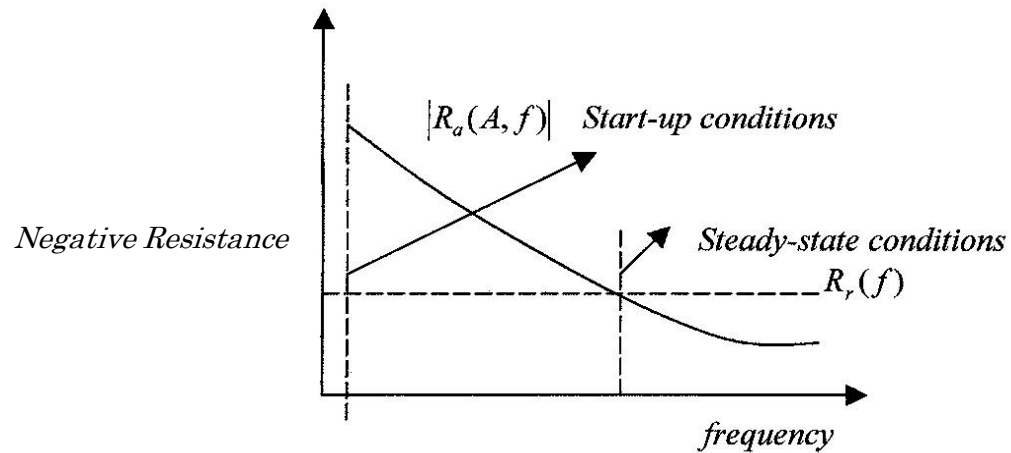This Figure illustrates the start and steady-state oscillation conditions.



A typical start and steady-state oscillation conditions.

$R_a(A, f)$ is the starting negative Resistance, which gets lower as the amplitude increases.

Therefore, feedback must be sufficient to maintain enough negative resistance to sustain oscillating.

Y_{21} Large Signal Calculation

$$Y_{21} = \frac{I_{1peak}}{V_{1peak}} \Big|_{\text{fundamental-frequency}}$$

$$I_1|_{n=1} = I_{dc} \left[1 + 2 \sum_1^{\infty} \frac{I_1(x)}{I_0(x)} \cos(wt) \right] \Rightarrow I_{1peak} = 2I_{dc} \frac{I_1(x)}{I_0(x)}$$

x = normalized drive level

$$V_1|_{peak} = \frac{kT}{q} x$$


$$Y_{21}|_{\text{large-signal}} = G_m(x)$$

$$Y_{21}|_{\text{small-signal}} = \frac{I_{dc}}{kT/q} = g_m$$


$$Y_{21}|_{\text{large-signal}} = G_m(x) = \frac{qI_{dc}}{kTx} \left[\frac{2I_1(x)}{I_0(x)} \right]_{n=1} = \frac{g_m}{x} \left[\frac{2I_1(x)}{I_0(x)} \right]_{n=1}$$

$$\frac{[Y_{21}|_{\text{large-signal}}]_{n=1}}{[Y_{21}|_{\text{small-signal}}]_{n=1}} = \frac{G_m(x)}{g_m} \Rightarrow \frac{2I_1(x)}{xI_0(x)}$$

$$|Y_{21}|_{\text{small-signal}} > |Y_{21}|_{\text{large-signal}} \Rightarrow g_m > G_m(x)$$

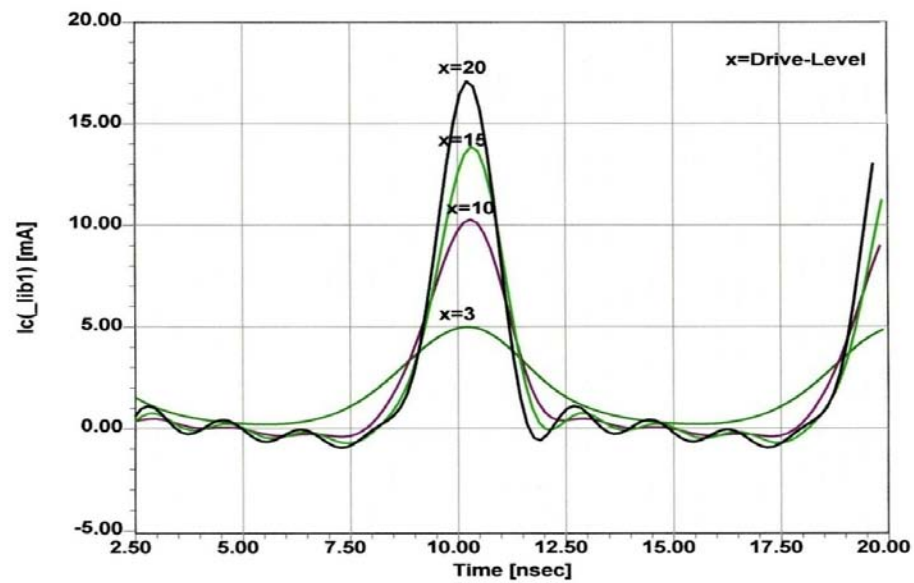


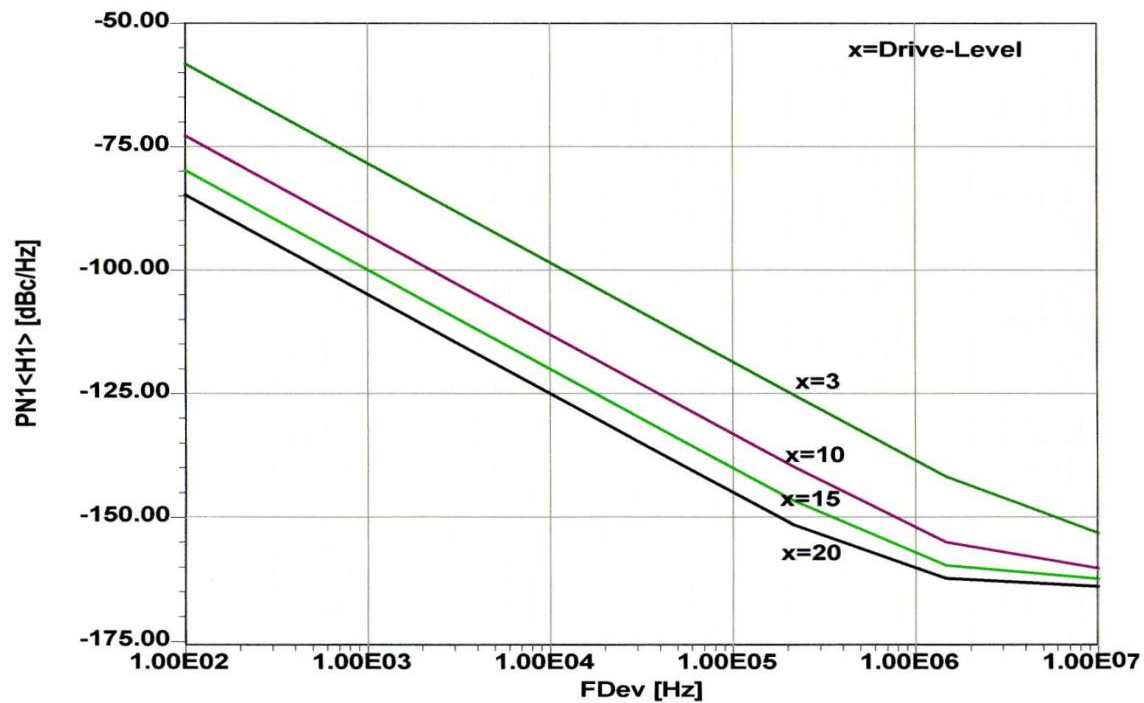Plot shows the collector current as a function of time with respect to normalized base drive Voltage x .





A typical phase noise plot of LC-based 1GHz oscillator as a function of x

GaAsOsc

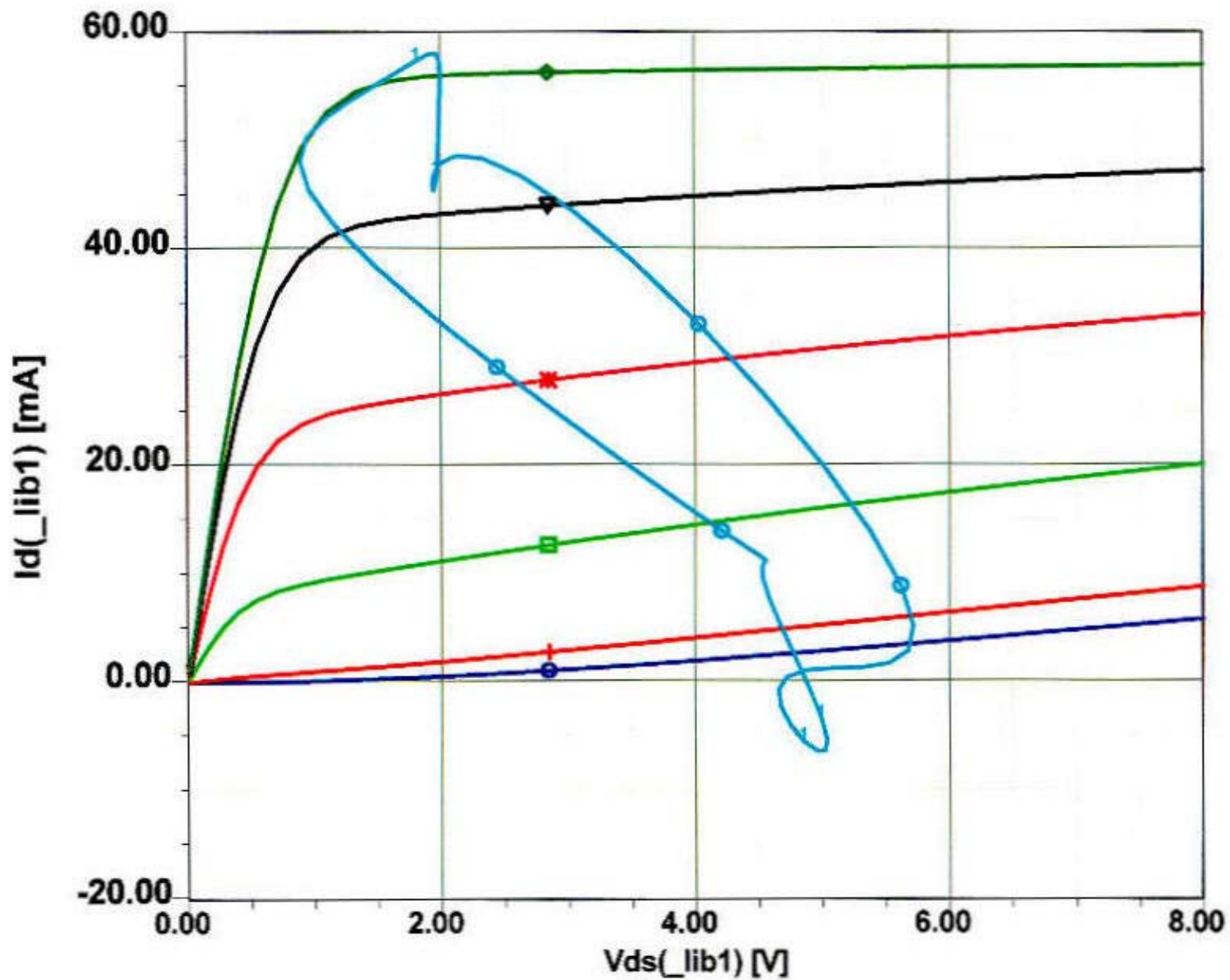

DiodeOsc

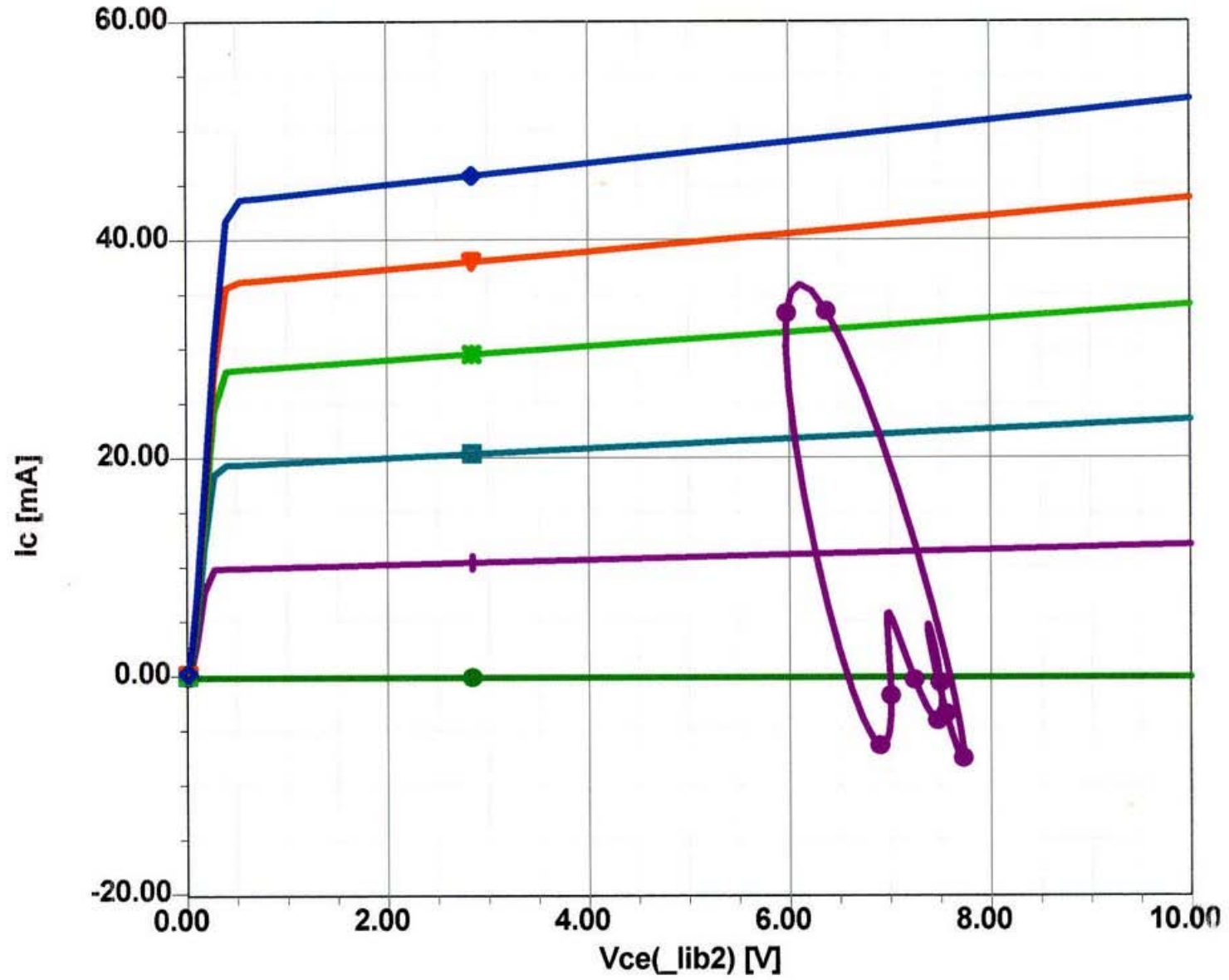

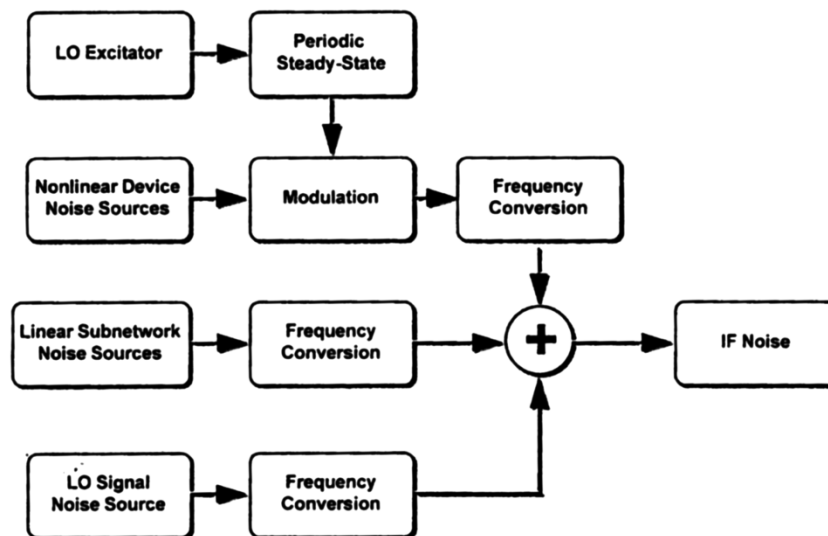

A typical block diagram where oscillator acts like a mixer.


The resulting phase noise in linear terms can be calculated as

$$\mathcal{L}(f_m) = \frac{1}{2} \left[1 + \frac{\omega_o^2}{4\omega_m^2} \left(\frac{P_{in}}{\omega_o W_e} + \frac{1}{Q_{uni}} + \frac{P_{sig}}{\omega_o W_e} \right)^2 \right] \left(1 + \frac{\omega_c}{\omega_m} \right) \frac{FkT_o}{P_{sav}}$$

This equation is the linear Leeson equation, with the pushing effect omitted and the flicker term added by Dieter Scherer (Hewlett Packard, about 1975); the final version with the pushing (supply voltage dependency VCO effect added by Rohde 2004), is

$$\mathcal{L}(f_m) = 10 \log \left\{ \left[1 + \frac{f_0^2}{(2f_m Q_L)^2} \right] \left(1 + \frac{f_c}{f_m} \right) \frac{FkT}{2P_{sav}} + \frac{2kTRK_0^2}{f_m^2} \right\}$$

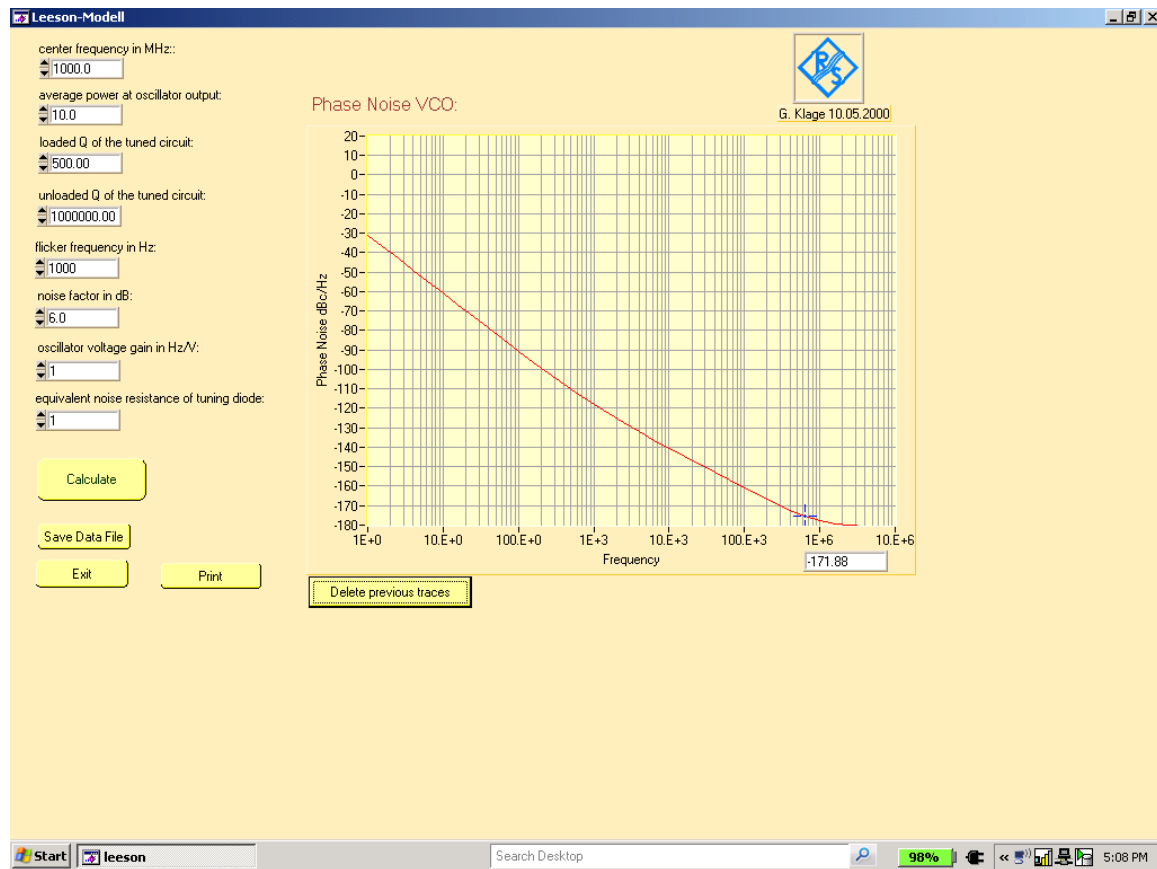This pushing also applies to the VCO case.



A typical phase noise plot for an ideal 1 GHz oscillator phase noise of about -140 dBc/Hz at offset of 10 kHz offset, assuming unloaded Q of 1 million loaded Q of 500, noise factor 6 dB, flicker frequency 1kHz, oscillator voltage gain 1Hz/V, equivalent noise resistance of tuning diode 1Ohm and average power at oscillator output 10 dBm. No diode contribution

Non-Linear Oscillator Equation

$$L \frac{di(t)}{dt} + (R_L - R_N(t))i(t) + \frac{1}{C} \int i(t) dt = e_N(t)$$

This is a nonhomogeneous differential equation, which can be simplified to [1, Ch-8, pp. 159-232]

$$L \left[-I_1(t) \left(\omega + \frac{d\varphi_1(t)}{dt} \right) \sin[\omega t + \varphi_1(t)] + \frac{dI_1(t)}{dt} \cos[\omega t + \varphi_1(t)] \right] + [(R_L - R_N(t))I(t)] +$$

$$\frac{1}{C} \left\{ \left[\frac{I_1(t)}{\omega} - \frac{I_1(t)}{\omega^2} \left(\frac{d\varphi_1(t)}{dt} \right) \right] \sin[\omega t + \varphi_1(t)] + \frac{1}{\omega^2} \left(\frac{dI_1(t)}{dt} \right) \cos[\omega t + \varphi_1(t)] \right\} = e_N(t)$$

Further

where $\overline{R_N(t)}$ is the average negative resistance under large signal condition.

$$\overline{R_N(t)} = \left[\frac{2}{T_0 I} \right] \int_{t-T_0}^t R_N(t) I(t) \cos^2[\omega t + \varphi] dt$$


And The SSB Phase Noise Is:

$$f(\omega) = 10 \times \log \left[k_0 + \frac{k^3 k_1 \left[\frac{Y_{21}^+}{Y_{11}^+} \right]^4 [y]^{4p}}{[Y_{21}^+]^6 [y]^{6q}} \left(\frac{1}{(y^2 + k)} \right) \left[\frac{[1+y]^2}{y^2} \right] \frac{Q_{\max}^2}{Q_0^2} \right]$$


Where

$$y = \frac{C_1}{C_2} \quad k_0 = \frac{kTR}{\omega^2 \omega_0^2 L^2 V_{cc}^2 C_2^2} \quad k_1 = \frac{qI_c g_m^2 + \frac{K_f I_b^{AF}}{\omega} g_m^2}{\omega^2 \omega_0^4 L^2 V_{cc}^2} \quad k_2 = \omega_0^4 (\beta^+)^2 \quad k = \frac{k_3}{k_2 C_2^2}$$

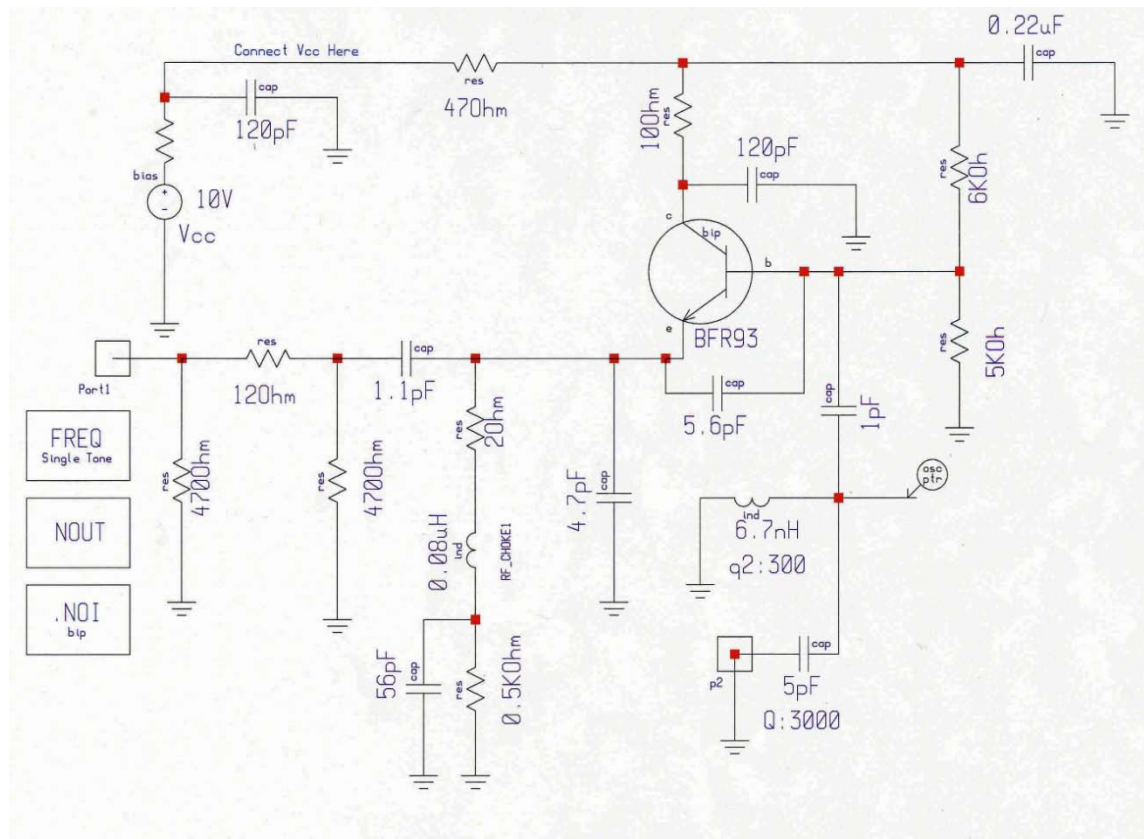
First ever complete and correct large signal phase noise calculation (Rohde 2004)



A typical 1 GHz oscillator circuit

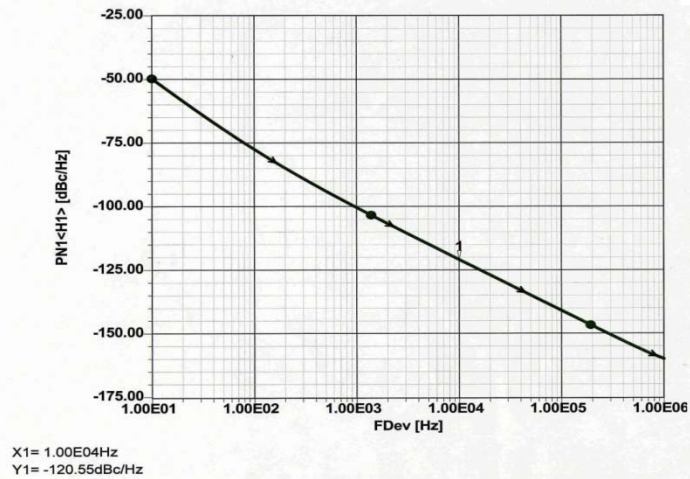

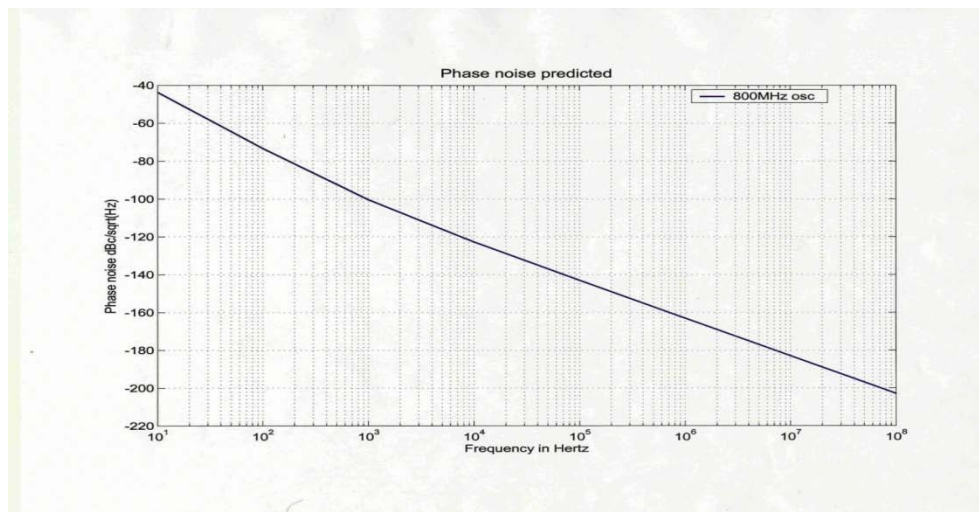A CAD Simulated (Ansoft Designer) phase noise plot for 1 GHz oscillator circuit




A CAD Simulated (MATLAB) phase noise plot for 1 GHz oscillator circuit


Multiple Magnetically Coupled Resonators

The quality factor of the coupled resonator network previously shown is given by

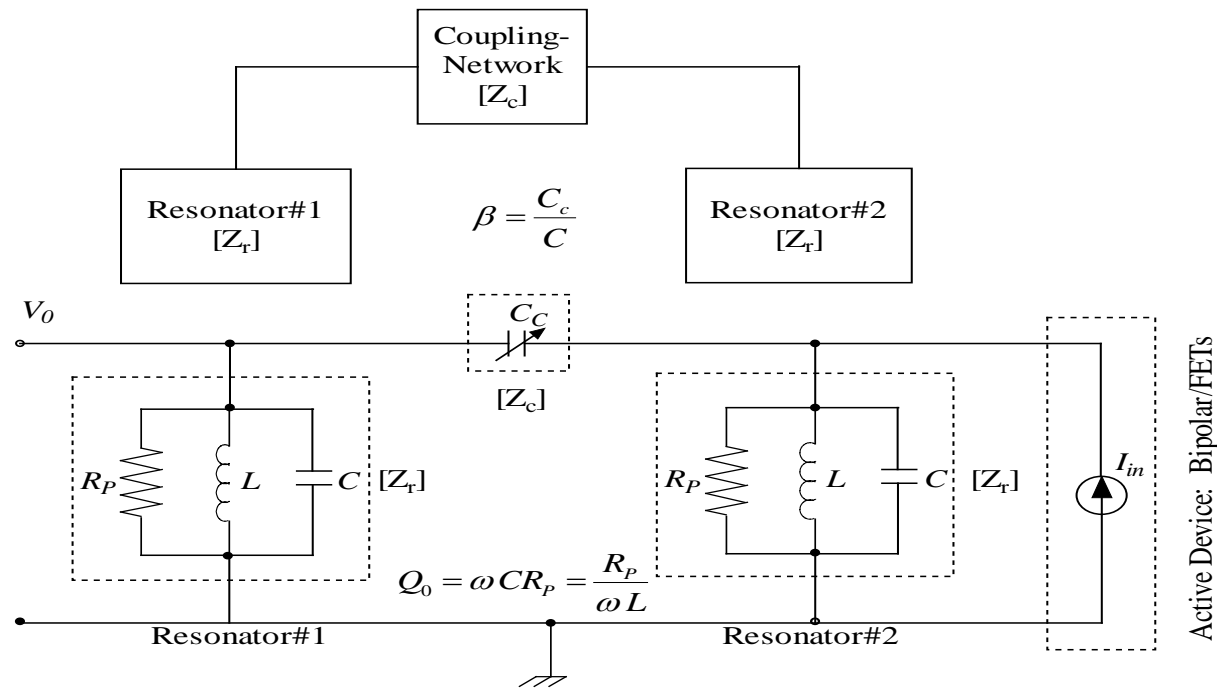
$$[Q_{coupled}(\omega)]_{\omega=\omega_0} = \frac{\omega_0}{2} \left[\frac{\partial \phi}{\partial \omega} \right] \Rightarrow \frac{2Q_0(1+\beta)}{(1+Q_0^2\beta^2)} \rightarrow \left[\frac{2Q_0(1+\beta)}{(1+Q_0^2\beta^2)} \right]_{\beta \ll 1} \approx 2Q_0$$




Capacitive coupled 2 resonators

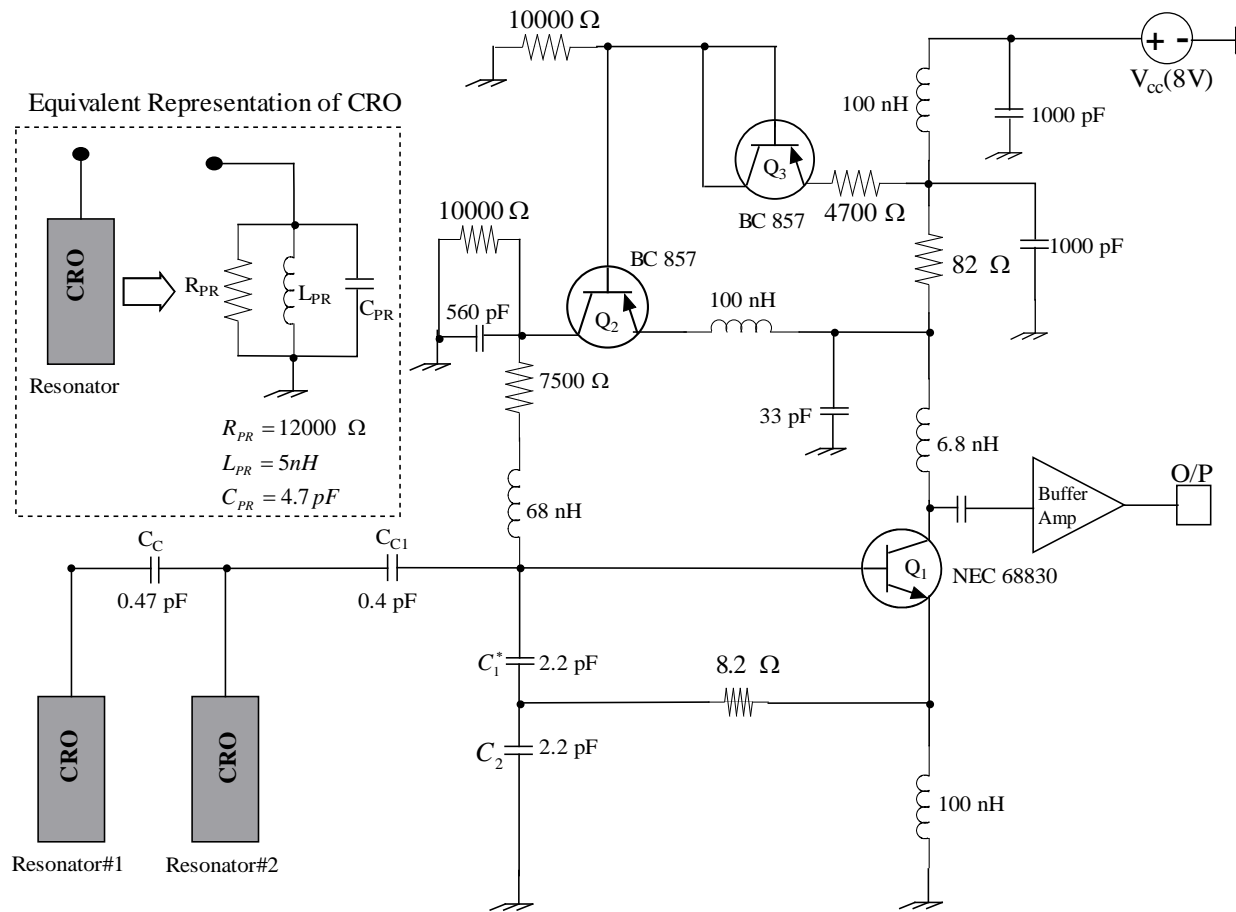


Circuit with Resonators

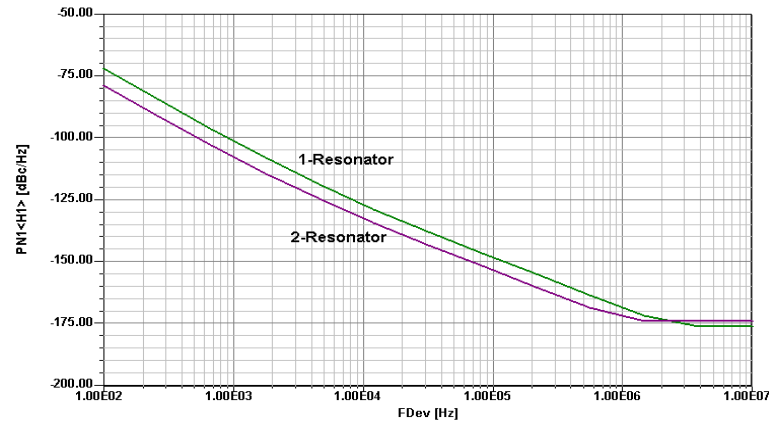

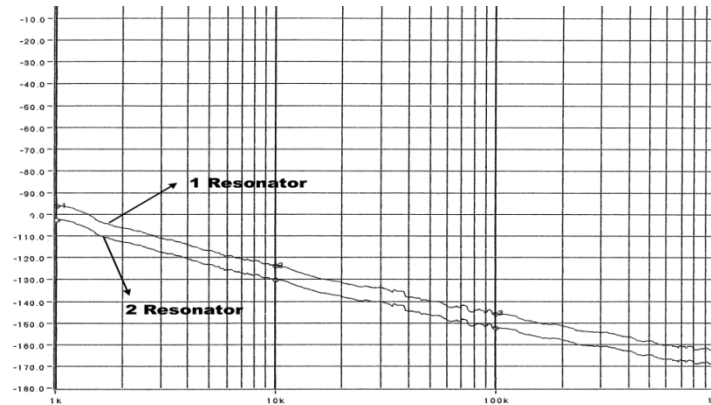
CAD simulated phase noise plot for the single resonator (1-resonator) and the identical coupled resonator (2-resonators)



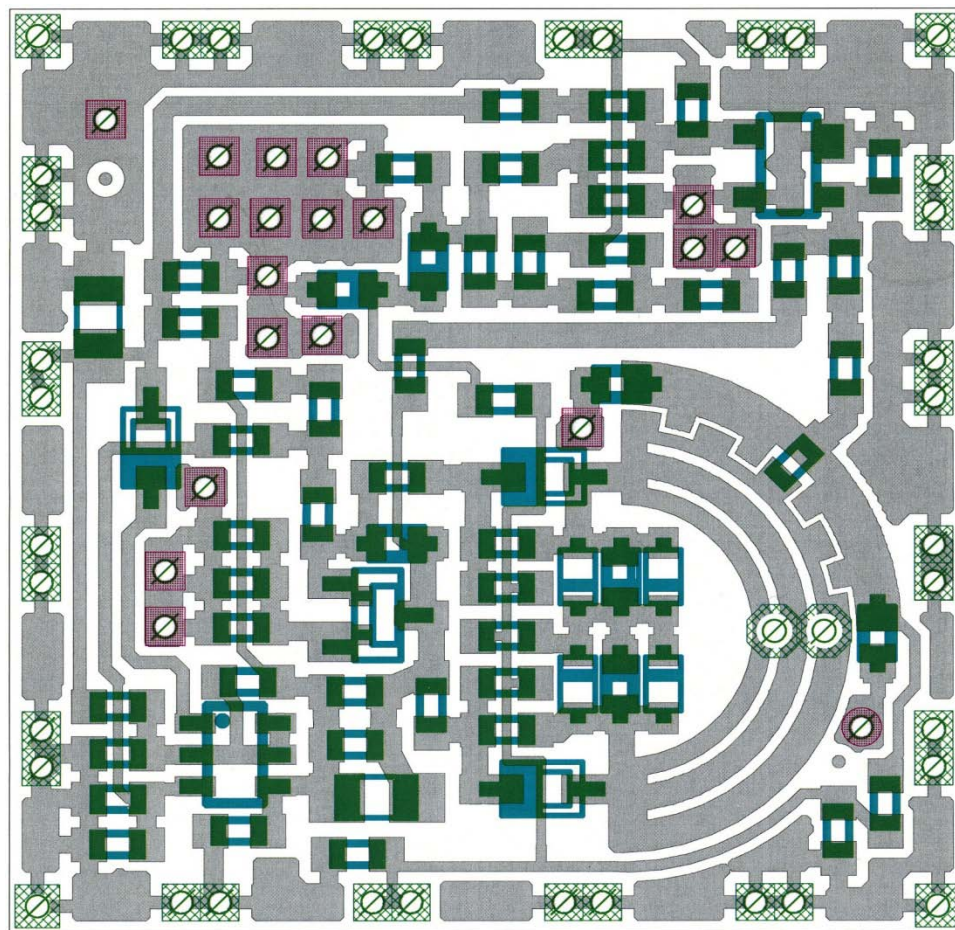Measured phase noise plots for the single resonator (1-resonator) and the identical coupled resonator (2-resonator)



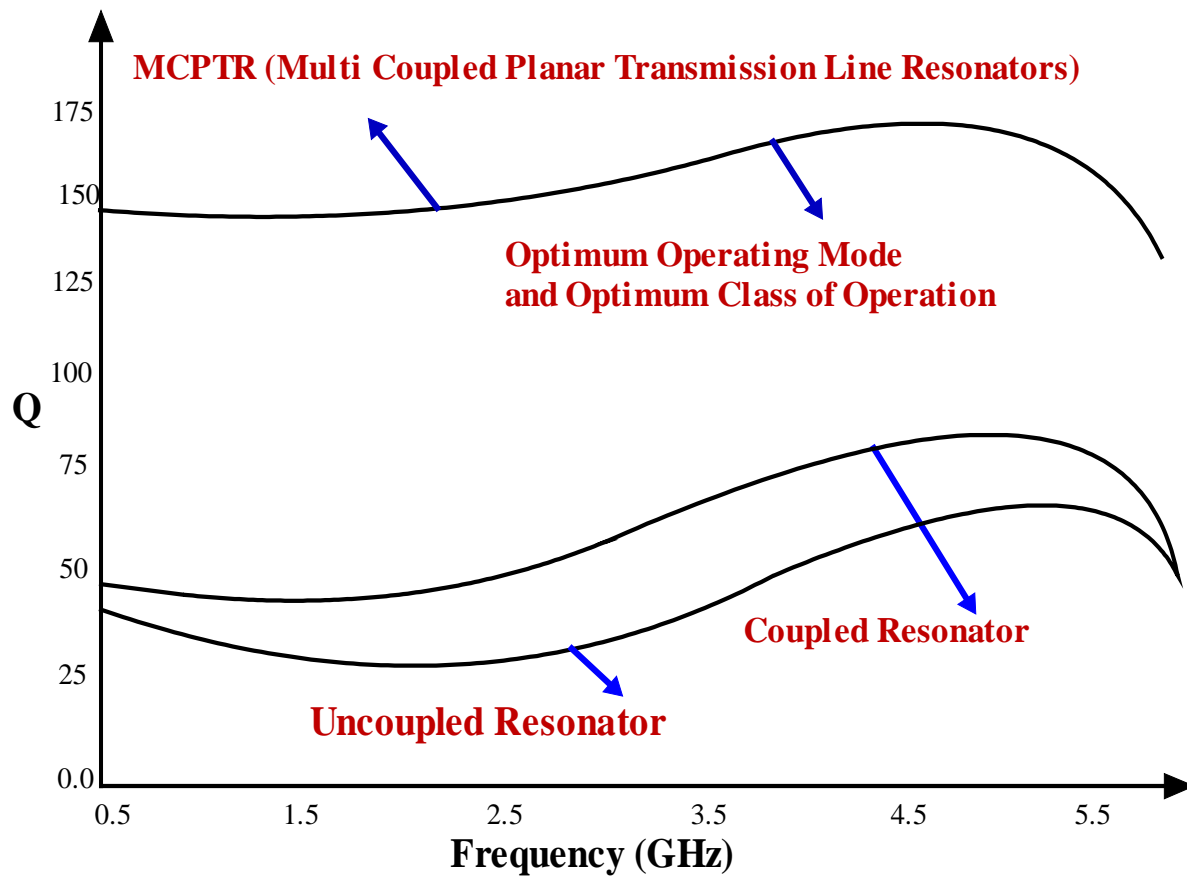Layout of the MCLR VCO (500MHz-2500MHz) (Patented)




Measured Q of resonators (uncoupled, coupled and MCLR)

Noise Optimization

$$\frac{d}{dm} \left[10 \log \left\{ \left[1 + \frac{f_0^2}{[2f_m Q_0 m(1-m)]^2} \right] \left(1 + \frac{f_c}{f_m} \frac{FkT}{2P_0} + \frac{2kTRK_0^2}{f_m^2} \right) \right\} \right]_{m_{opt}}$$


$$m_{opt} \rightarrow 0.5 \Rightarrow \left[\frac{d\phi}{d\omega} \right]_{\phi=\phi_{opt}} = \frac{Q_{unloaded}}{\omega_0}$$

Coupling Factor = 0.5

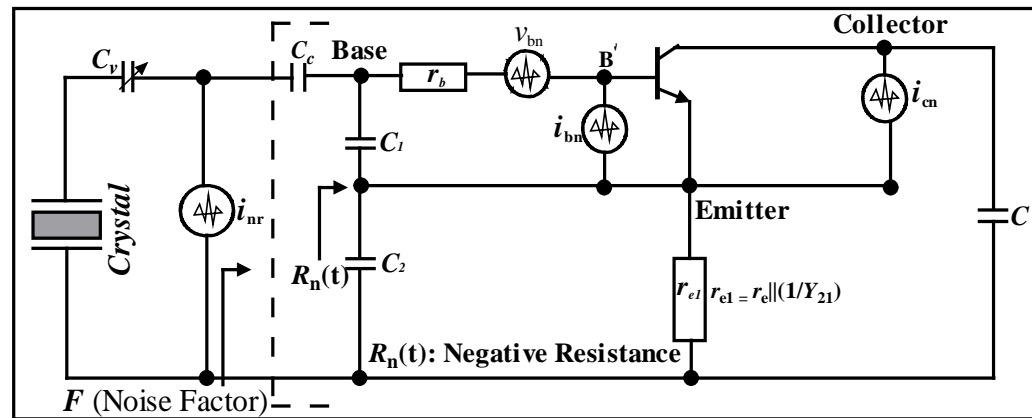


$$F = 1 + \frac{Y_{21}^+ C_2 C_c}{(C_1 + C_2) C_1} \left[r_b + \frac{1}{2r_e} \left(r_b + \frac{(C_1 + C_2) C_1}{Y_{21}^+ C_2 C_c} \right)^2 \left(\frac{1}{\beta^+} + \frac{f^2}{f_T^2} \right) + \frac{r_e}{2} \right]$$


Noise Factor of Oscillator

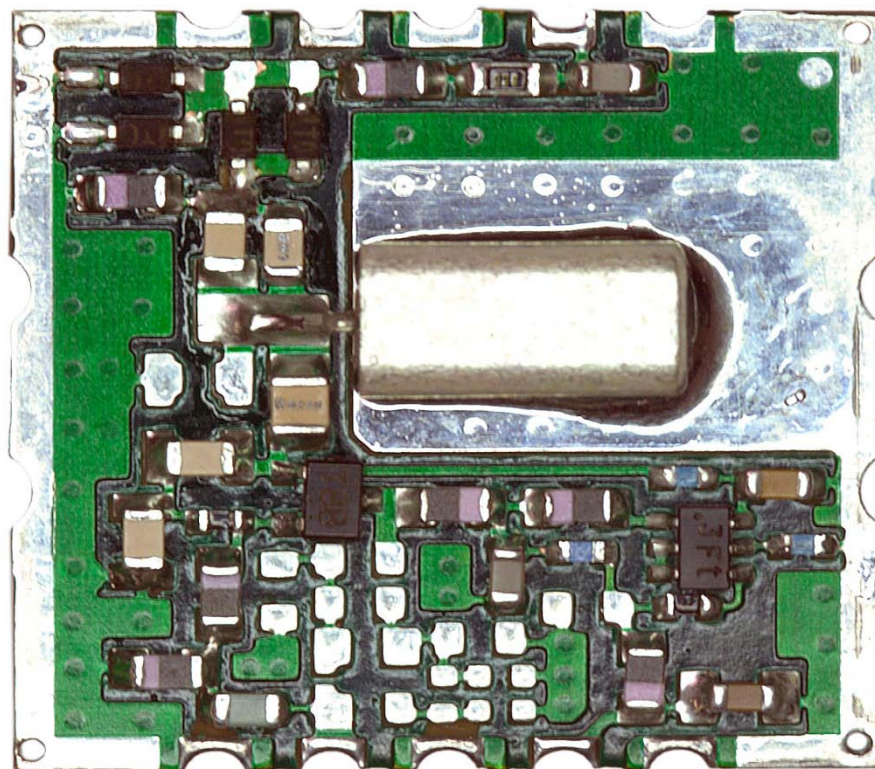

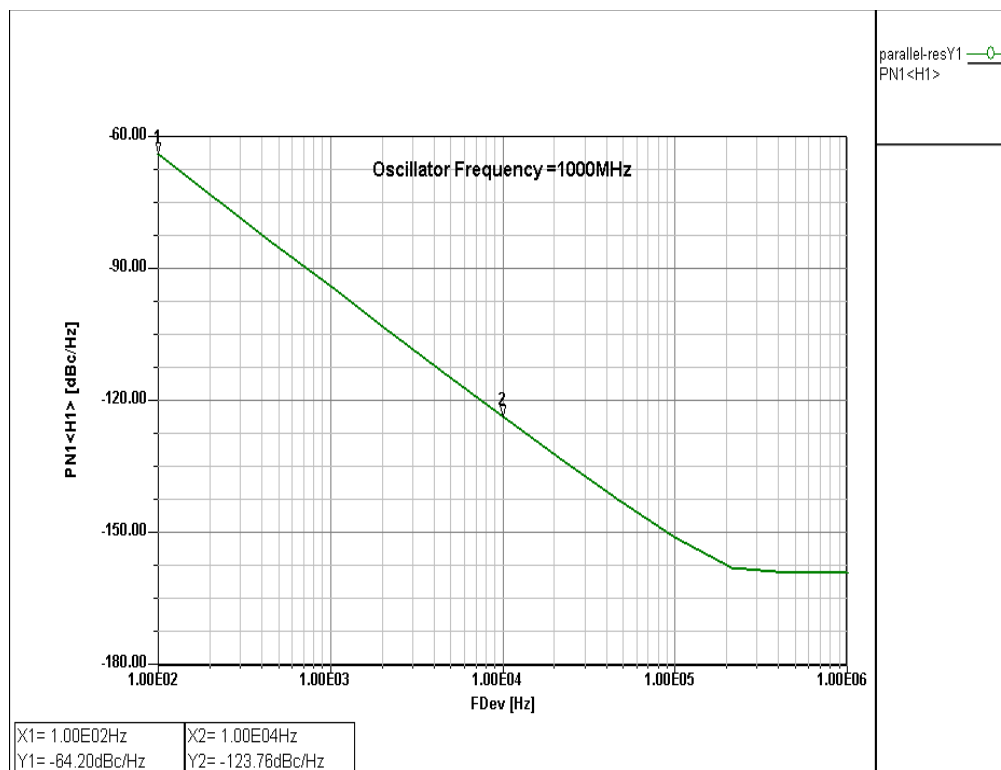
Layout of 1GHz Colpitts oscillator (Ceramic resonator oscillator)




Simulated phase noise plot of for CRO

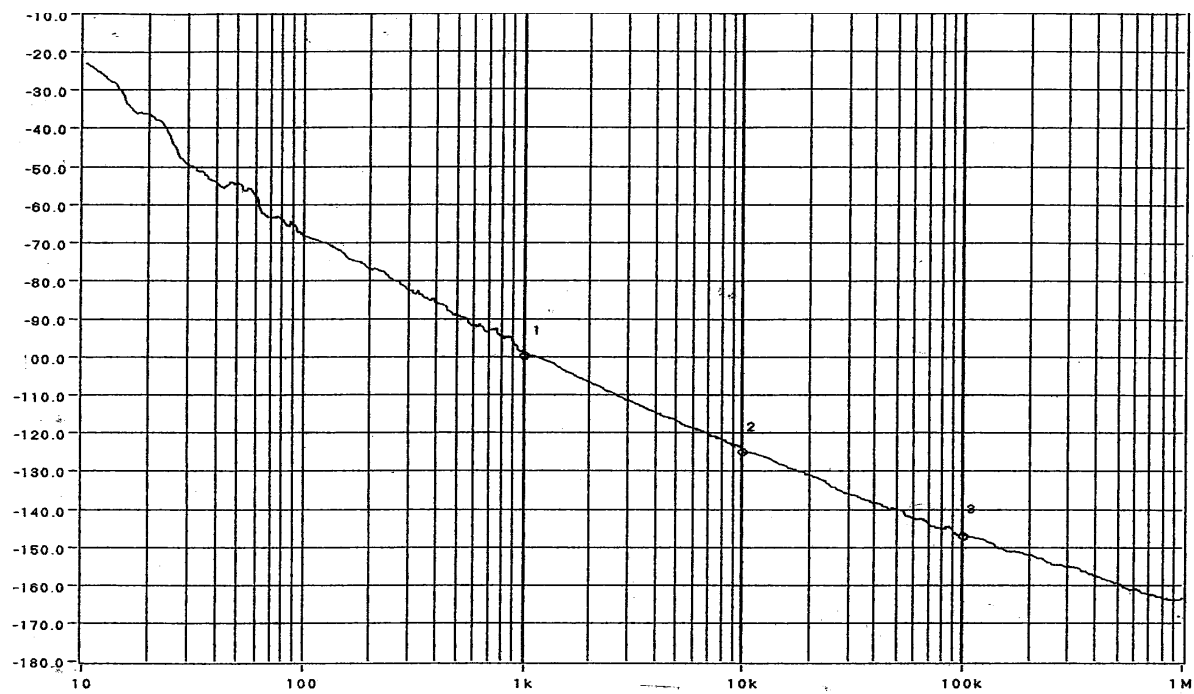


Measured phase noise plot of the CRO

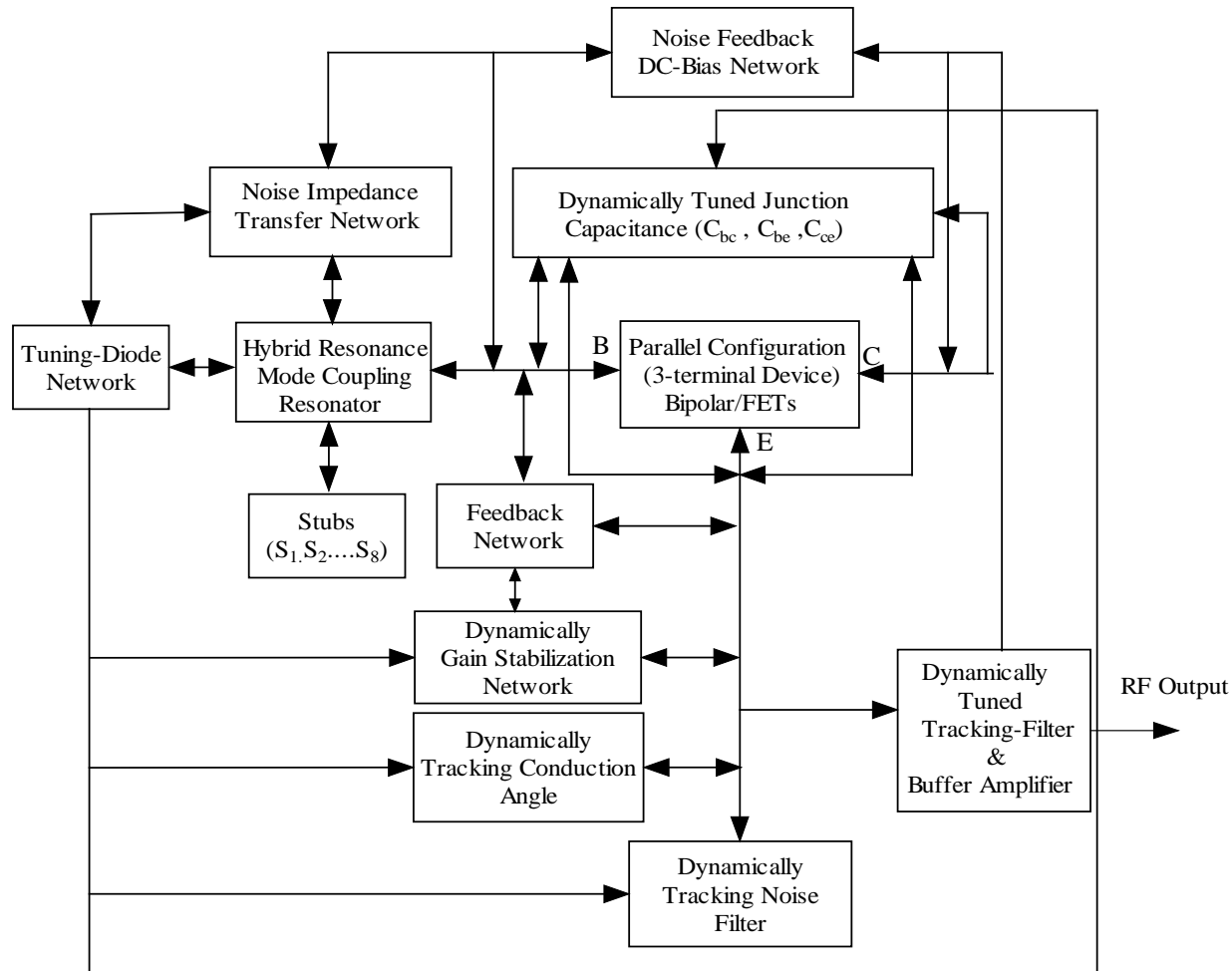

Block diagram of a user-defined MCLR VCO

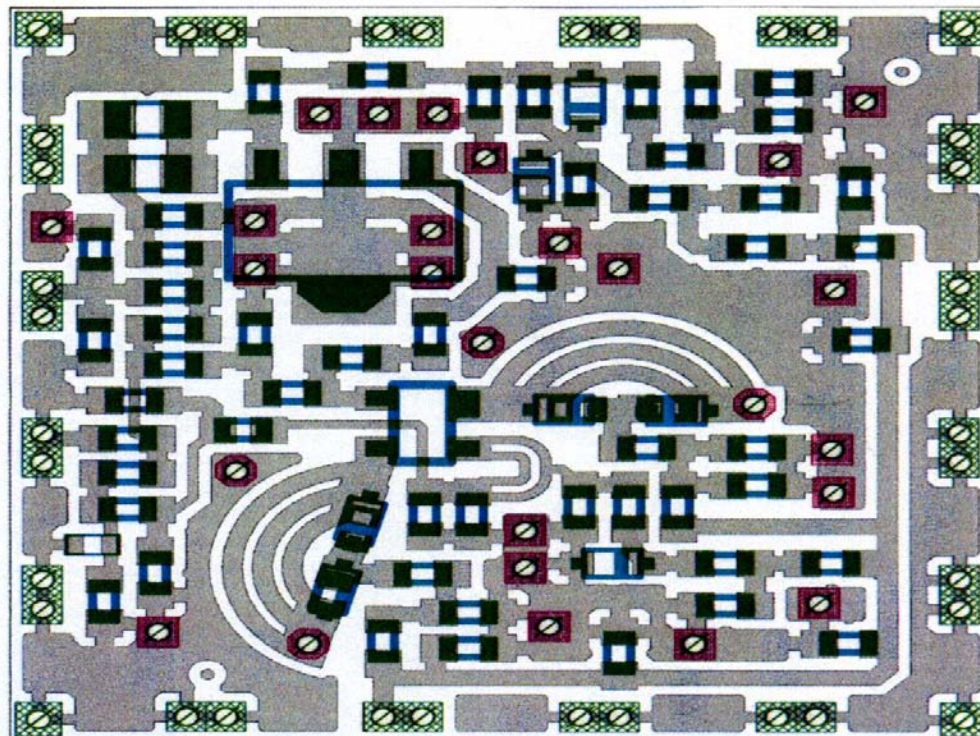

Layout of dual-band RCO (Patent pending)

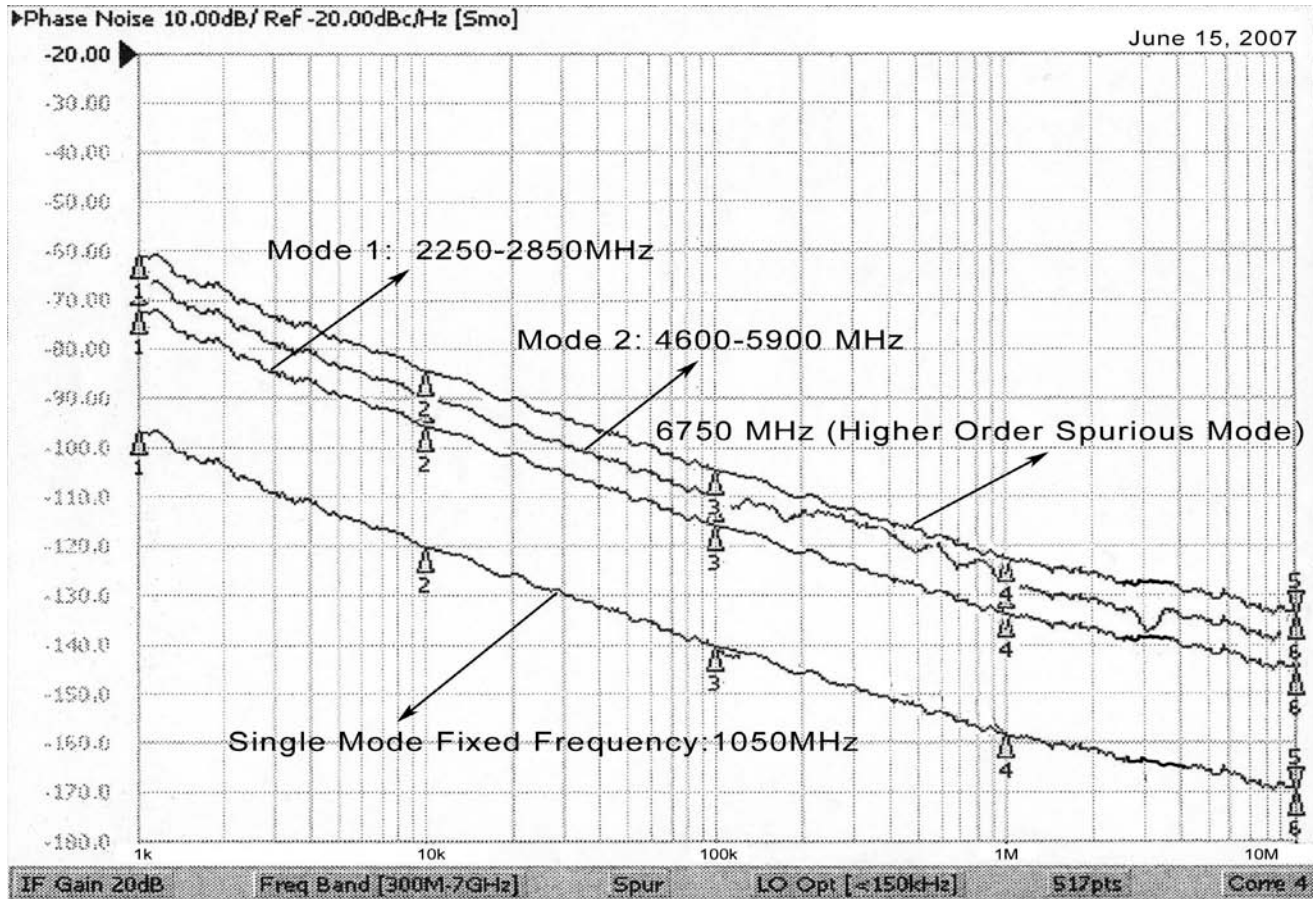

Phase noise plot of the dual-band VCO

Thank You



Are there any questions?